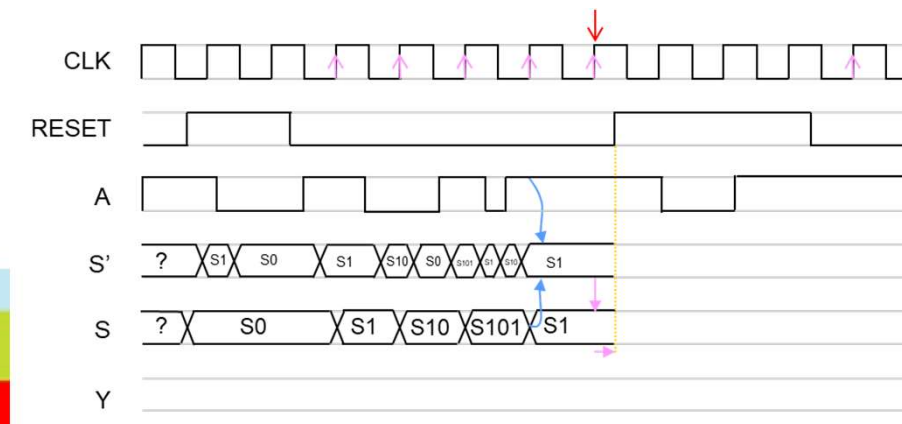


CEU

Universidad  
San Pablo

## Timing diagrams of Finite State Machines



**Gabriel Caffarena**


Departamento de Tecnologías de Información

Universidad San Pablo CEU

Curso 2018/2019
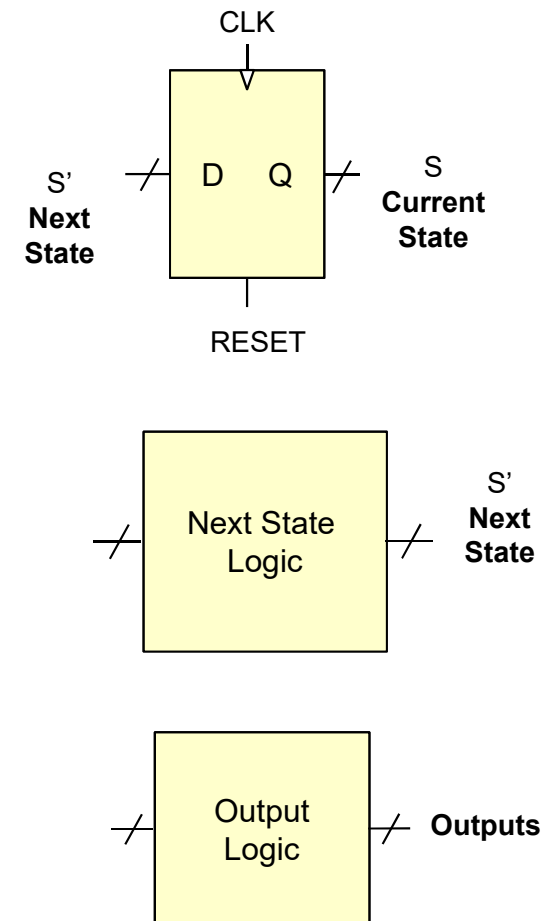
# Finite State Machine (FSM)


- Used to generate a sequence of control signals that react to the value of inputs
  - The sequence is synchronous with a periodic clock signal
- Consists of:
  - State register that
    - Store the current state and
    - Load the next state at the clock edge
  - Combinational logic that
    - Computes the next state
    - Computes the outputs



# Finite State Machines (FSMs)


- Next state is determined by the current state and the inputs
- There are two types of finite state machines depending on the output logic:
  - **Moore FSM:** the outputs depend **only** on the current state (Edward F. Moore, 1956)
  - **Mealy FSM:** outputs depend on the current state *and* the inputs (George H. Mealy, 1955)

## MOORE FSM

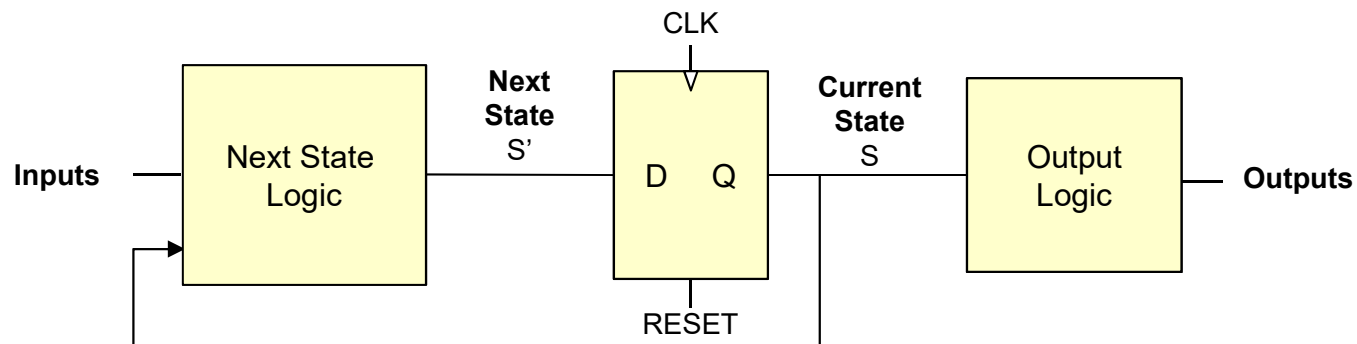

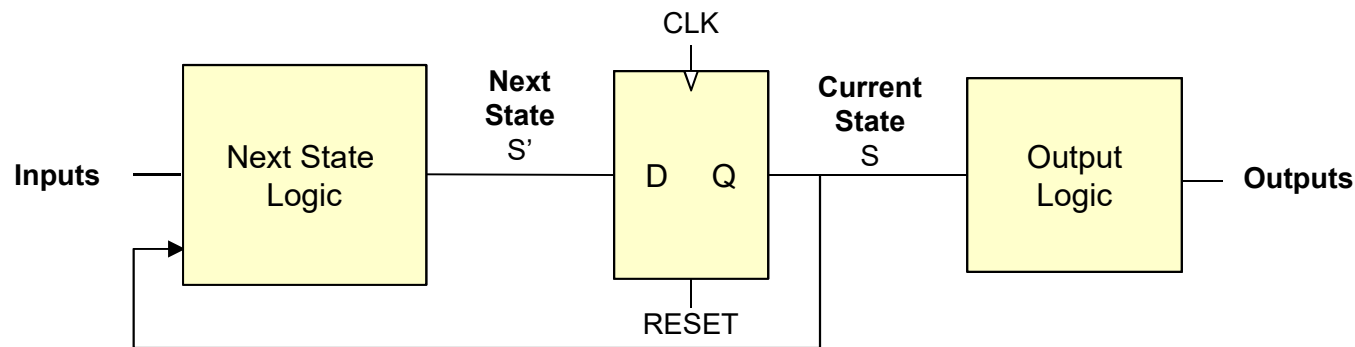
# Moore Finite State Machines

- Let's analyze the block diagram
  - The RESET signal resets the state to the initial state (i.e. S0)
  - When a clock Edge occurs  $S=S'$
  - The outputs are updated everytime S is updated
  - The next state S' is updated if S is update and/or the inputs change



 
# FSM example

- System that reads a binary sequence A and detect the pattern 101
- The end of one pattern can be the beginning of a new pattern




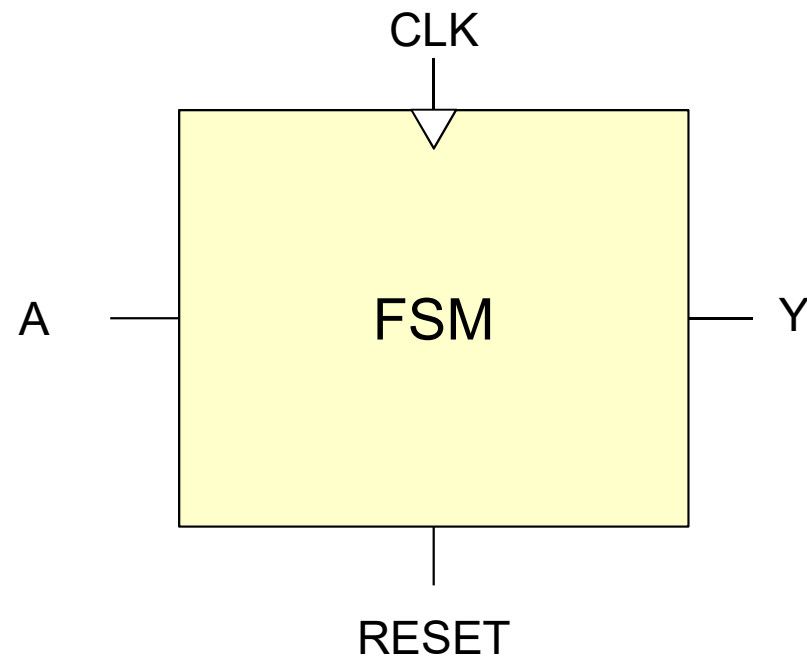- Inputs: *CLK*, *Reset*, *A*
- Outputs: *Y*
  - 1 if pattern found



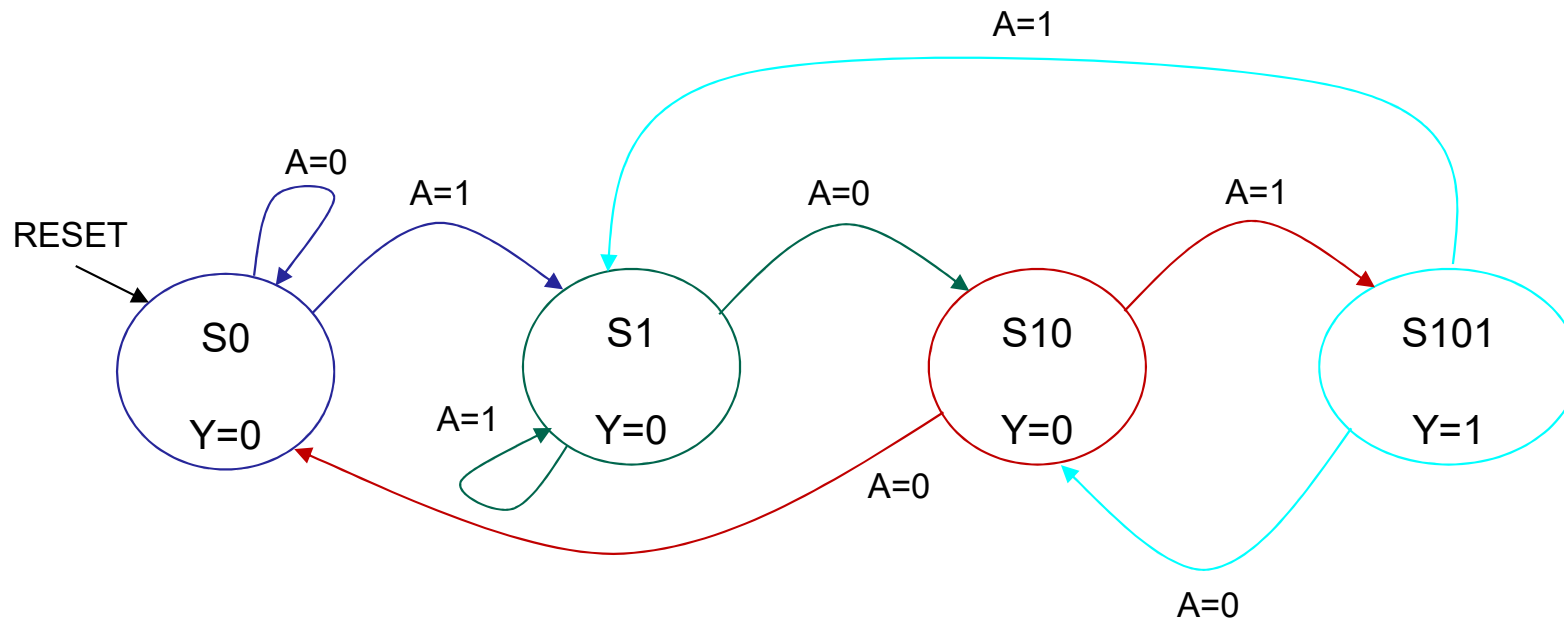
# FSM State Transition Diagram

- Moore FSM: outputs labeled in each state
- States: Circles
- Transitions: Arcs



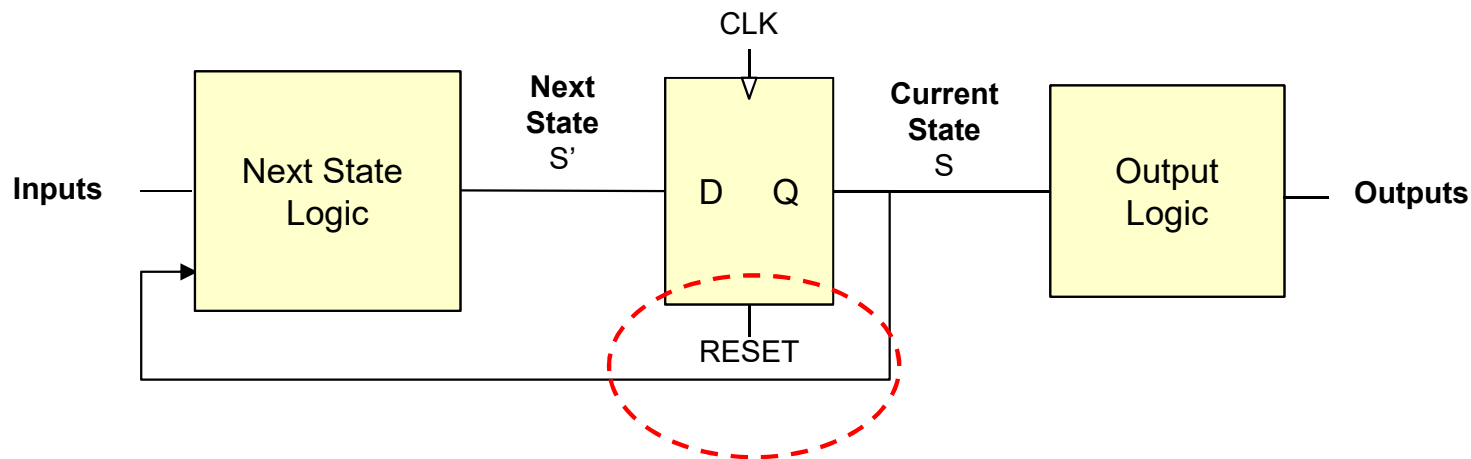
# FSM Timing Diagram: Steps

- Reset
  - We assume that the reset signal is active high, that is:
    - If  $RESET=1$  then the output of the register is all zeros, so  $S=S_0$ , being  $S_0$  the initial state.
    - IF  $RESET=0$  the value of the output of the register will be kept until a clock edge (transition from 0 to 1) occurs, and the value of  $S$  will be replaced by  $S'$  for a whole clock period


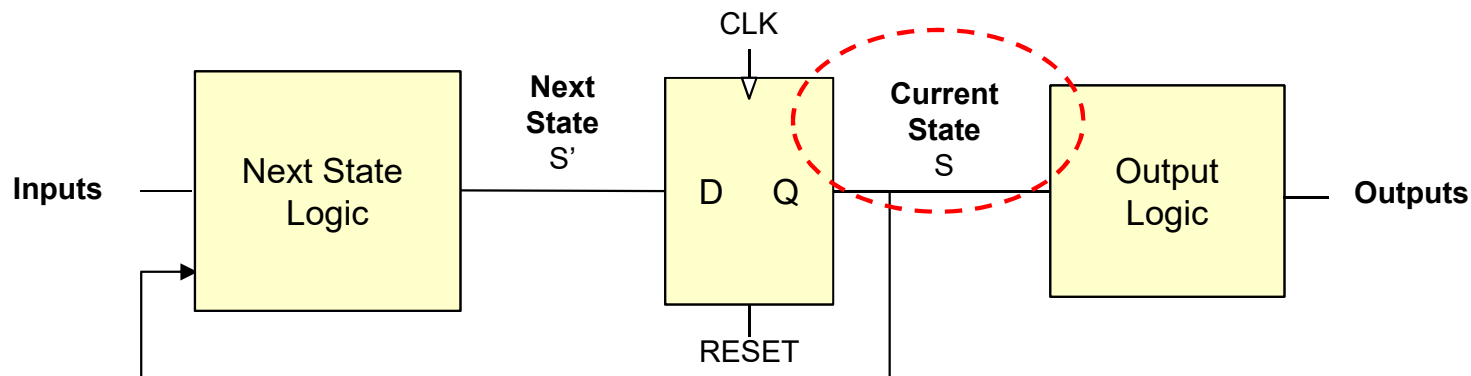
# FSM Timing Diagram: Steps


- Clock edge (assuming that RESET=0)
  - We assume that the register react to rising clock edges (edge from 0 to 1):
    - $S=S'$  just after the clock edge (there will be a minor delay due to the propagation time of the registers that we will consider negligible).





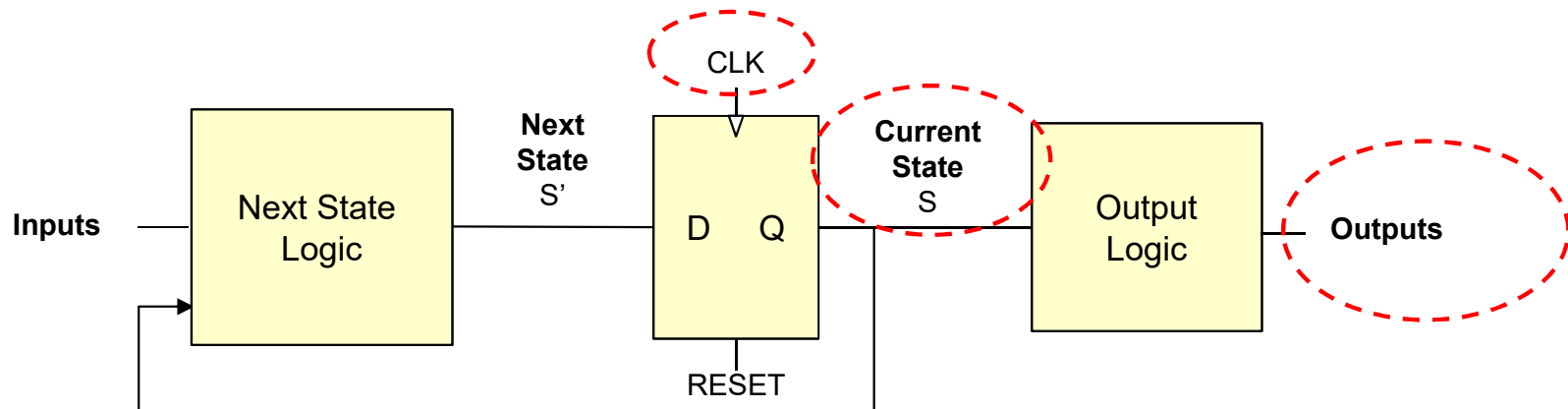
# FSM Timing Diagram: Steps

- After the clock edge (assuming that RESET=0)
  - If S changed then the outputs might change depending on the current state (see state transition diagram)
  - There will be a delay due to the propagation delay of the combinational logic of the “output logic” block



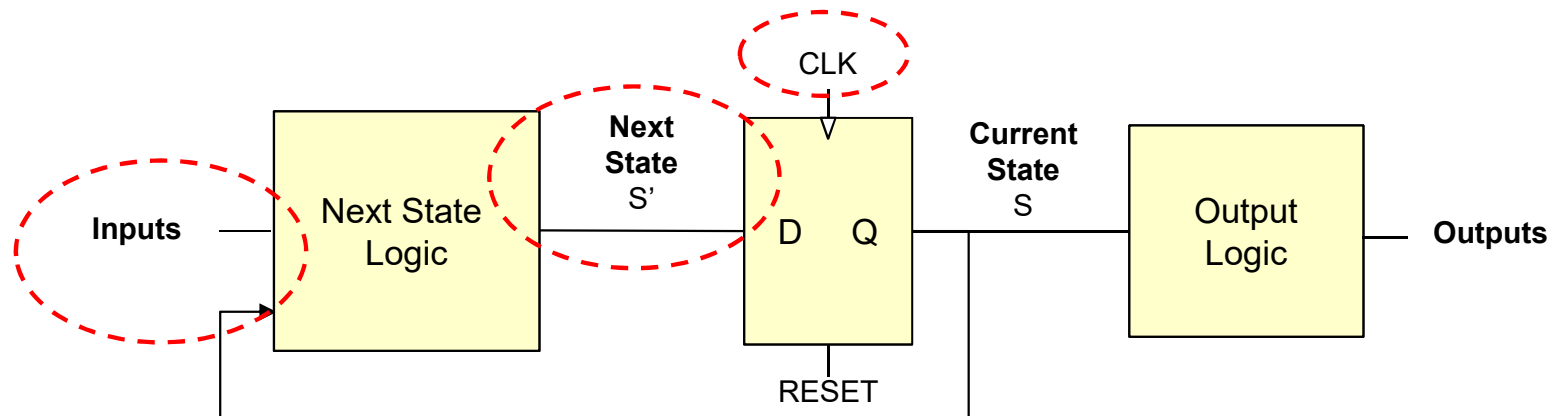
# FSM Timing Diagram: Steps

- After the clock edge (assuming that RESET=0)
  - If S changed then the next state S' might change depending on the values of S and the inputs (see state transition diagram)
  - The change will have a delay due to the propagation delay of the combinational logic of the “next state logic” block


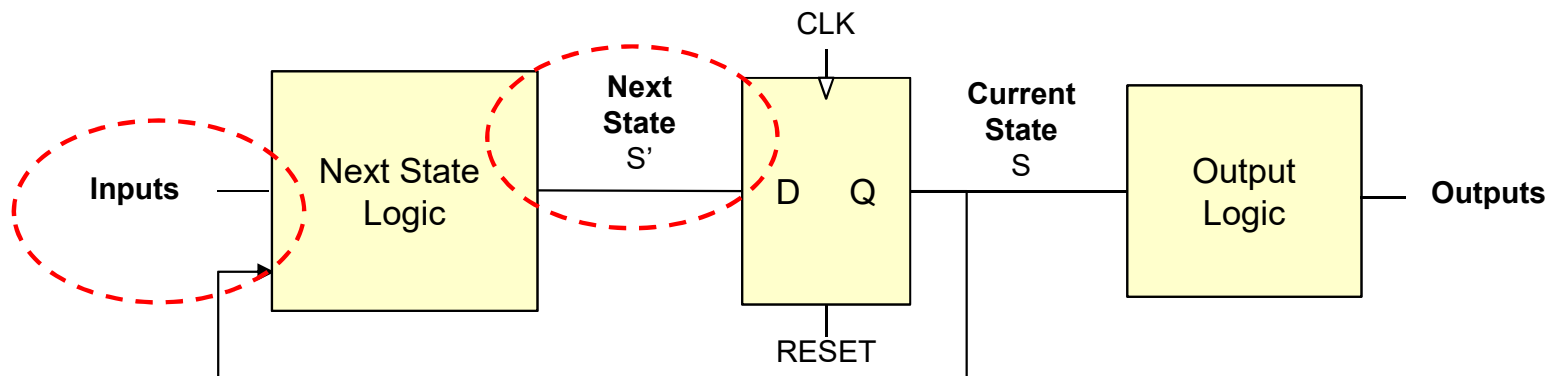
# FSM Timing Diagram: Steps




- Inputs
  - The inputs are not synchronized with the clock, so if the change  $S'$  might change depending on the values of  $S$  and the inputs (see state transition diagram)
  - The change will have a delay due to the propagation delay of the combinational logic of the “next state logic” block






# FSM Timing Diagram: Drawing the timing diagram

- In order to draw the timing diagram we require to specify the values of:
  - The clock and the reset signal
  - The inputs
- With that information and following the previous steps it will be possible to obtain the values of the outputs
  - It is necessary to obtain the value of  $S$ , which depends on the value of  $S'$
  - $S$  and  $S'$  must be part of the diagram
- Since the outputs are directly related to  $S$  we can leave them to the end and focus on  $S$  and  $S'$

 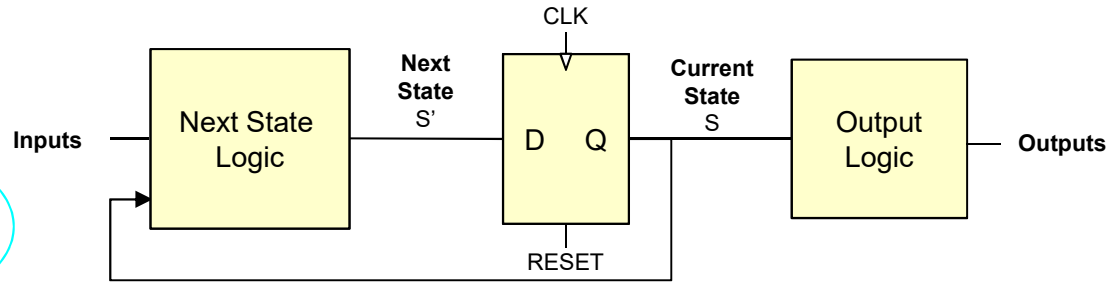
 
# FSM Timing Diagram: Drawing the timing diagram



  
 
# FSM Timing Diagram: Drawing the timing diagram


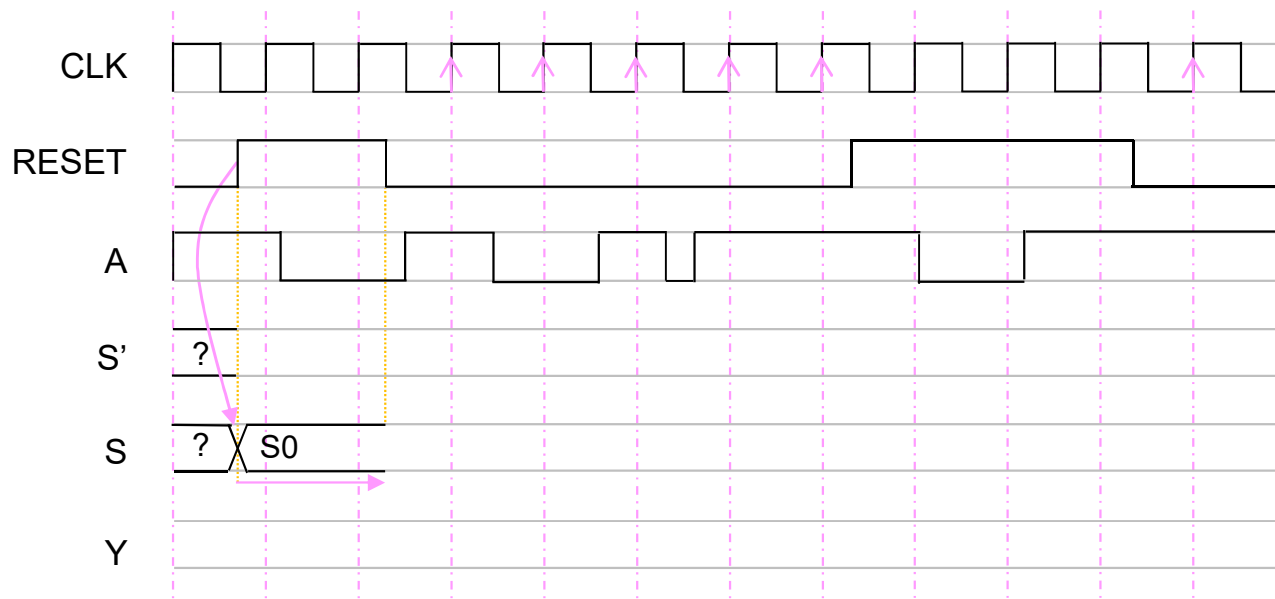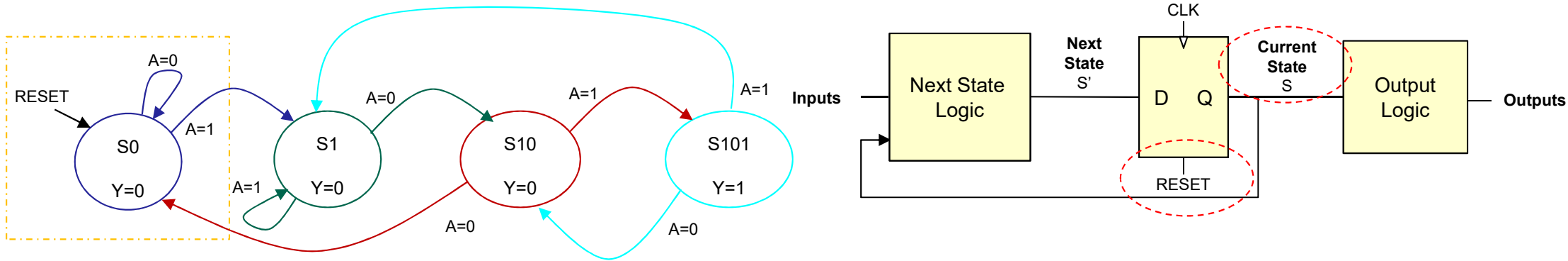
# FSM Timing Diagram: Drawing the timing diagram




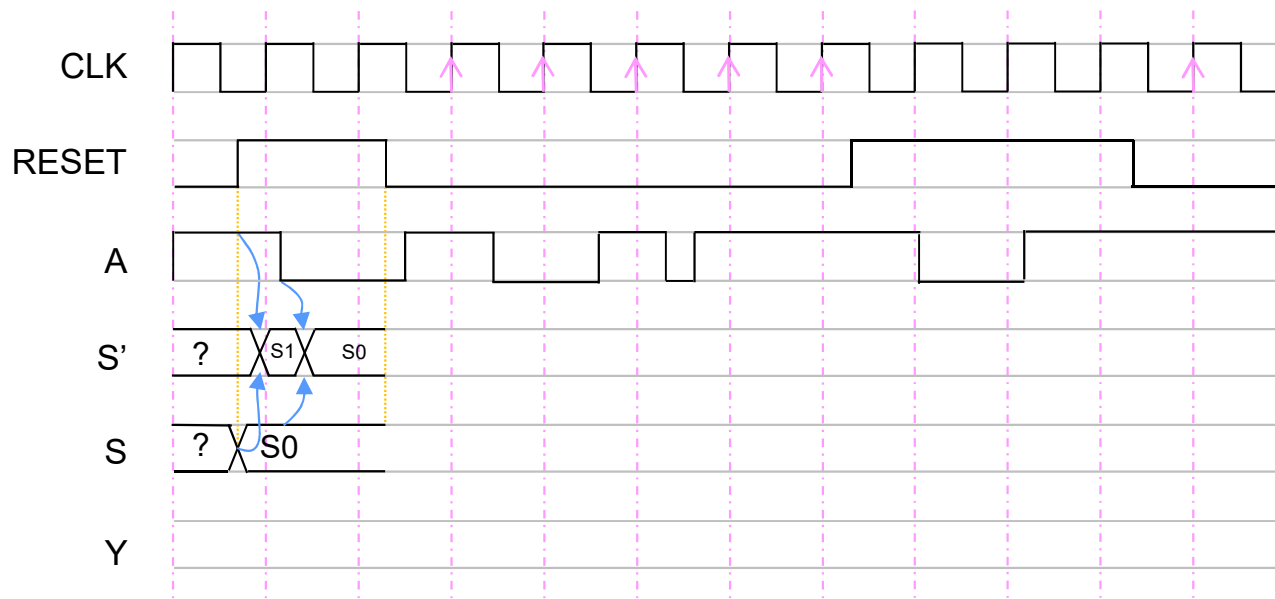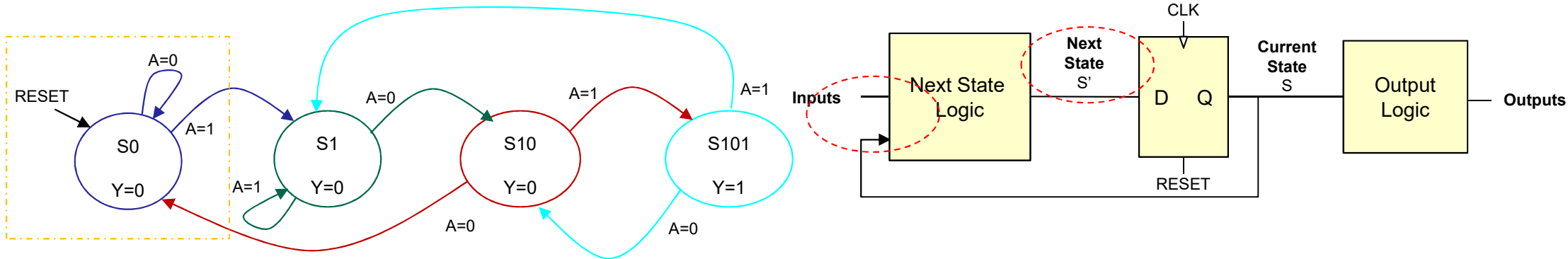
# FSM Timing Diagram: Drawing the timing diagram








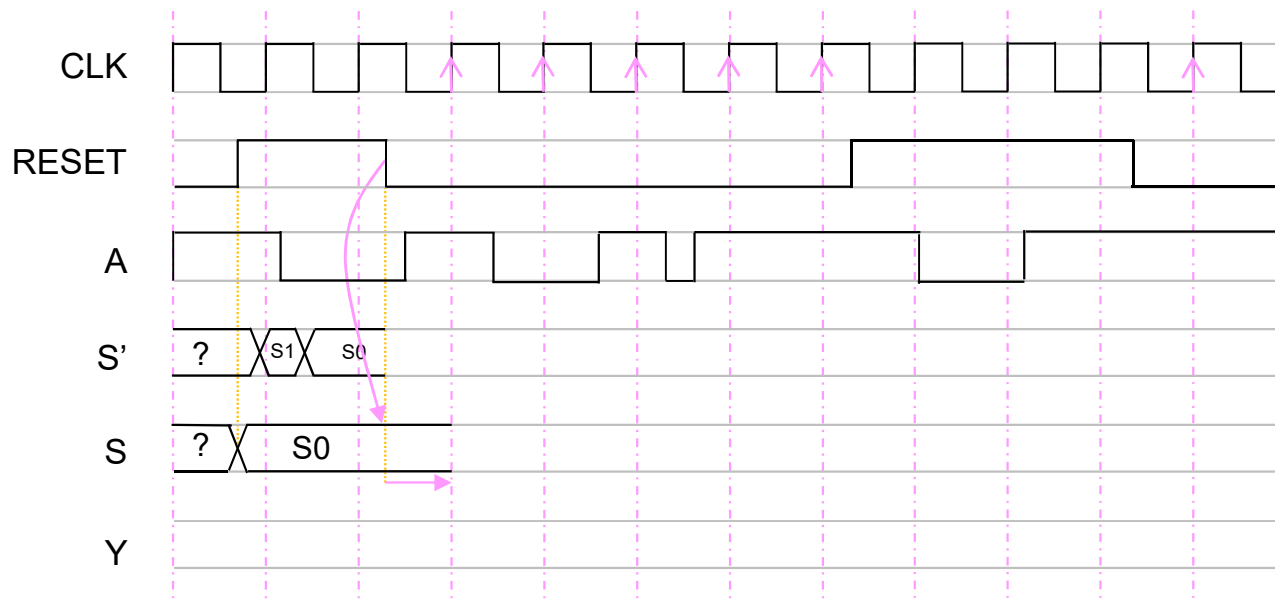
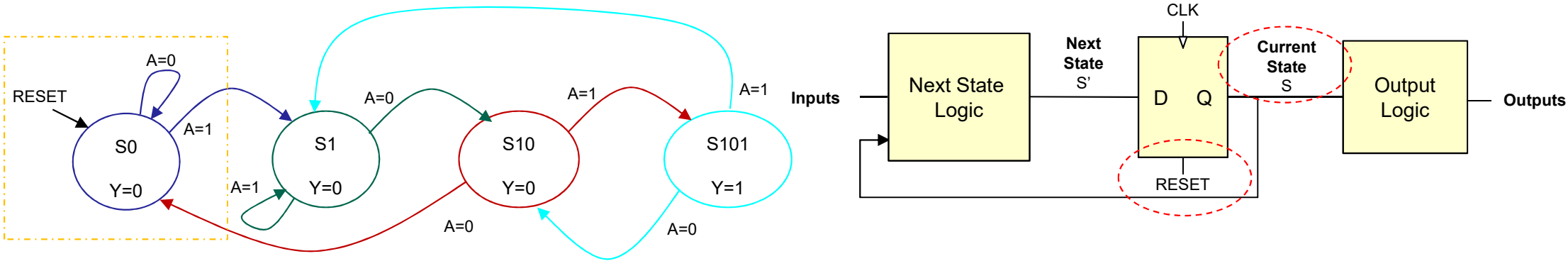
# FSM Timing Diagram: Drawing the timing diagram



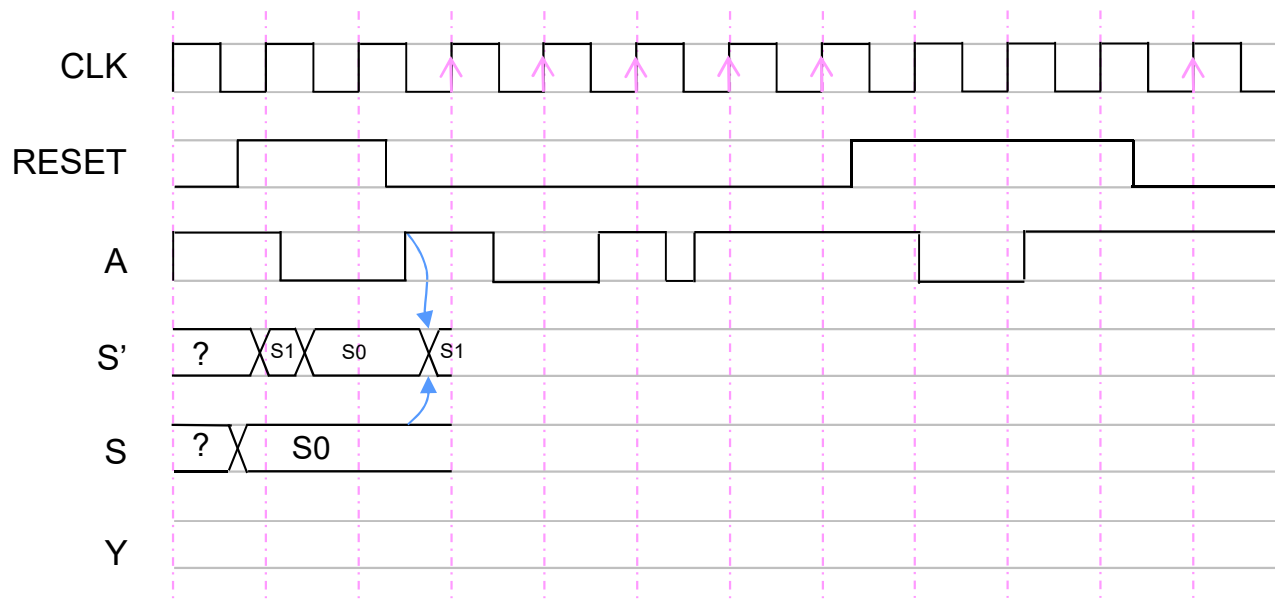
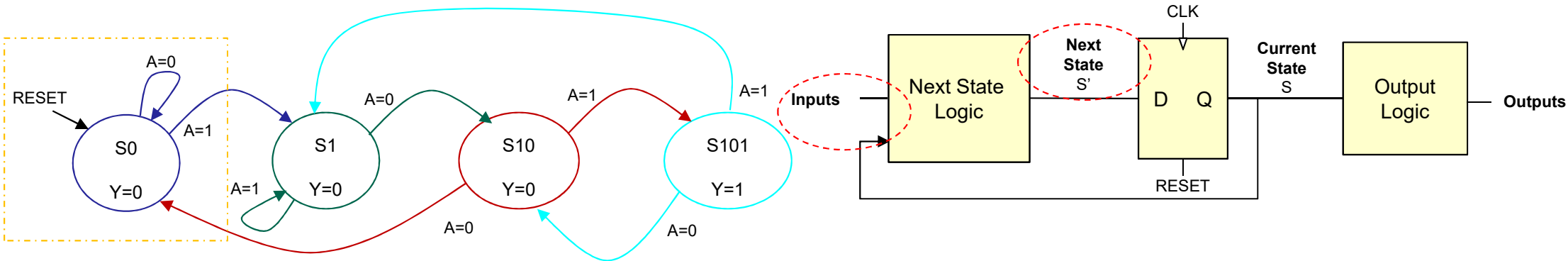
# FSM Timing Diagram: Drawing the timing diagram



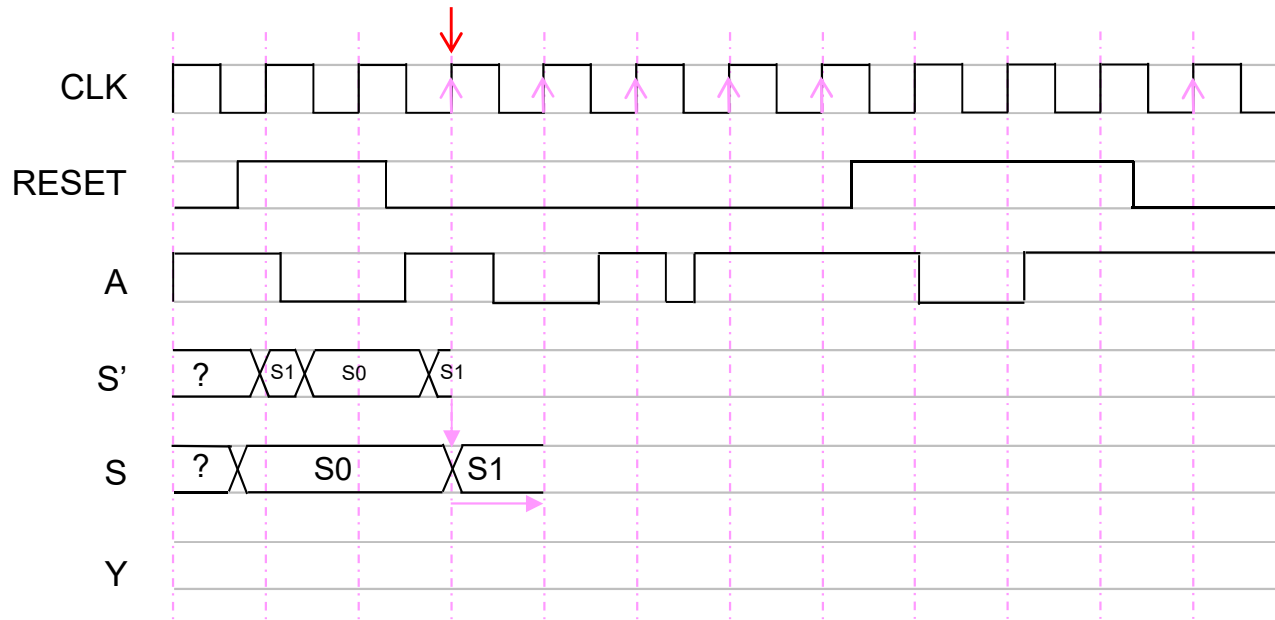
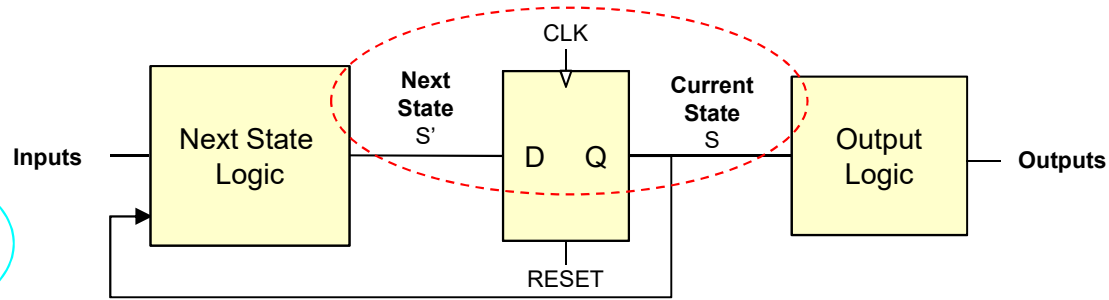
 
# FSM Timing Diagram: Drawing the timing diagram



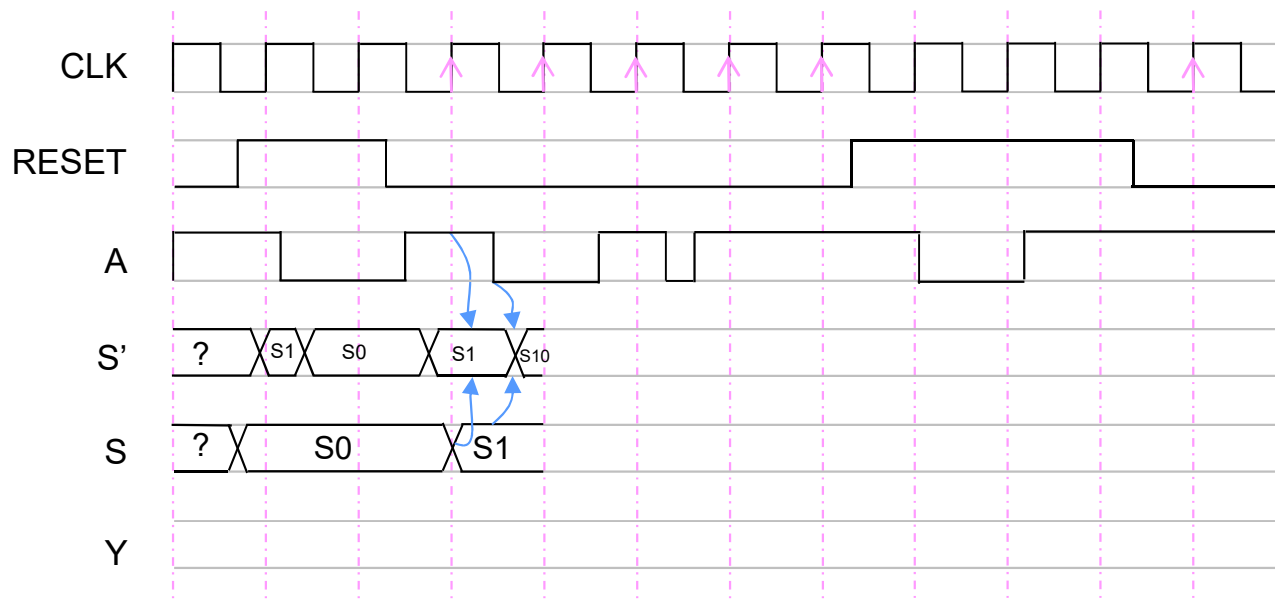
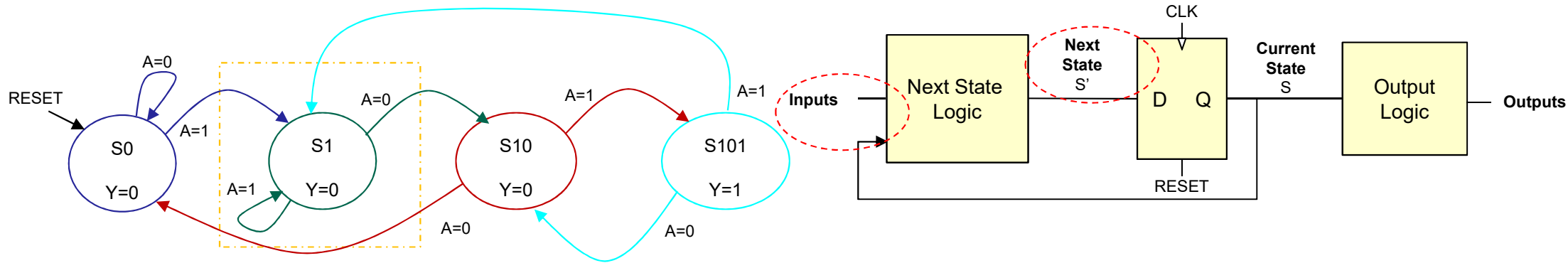
# FSM Timing Diagram: Drawing the timing diagram



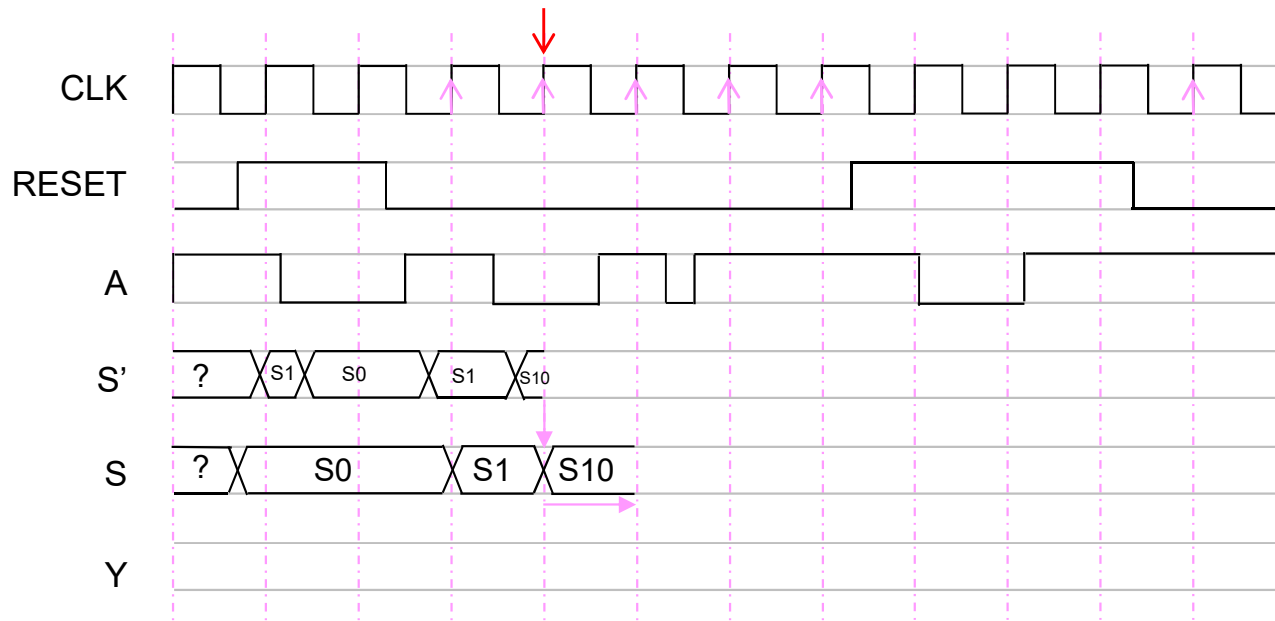
 
 
# FSM Timing Diagram: Drawing the timing diagram



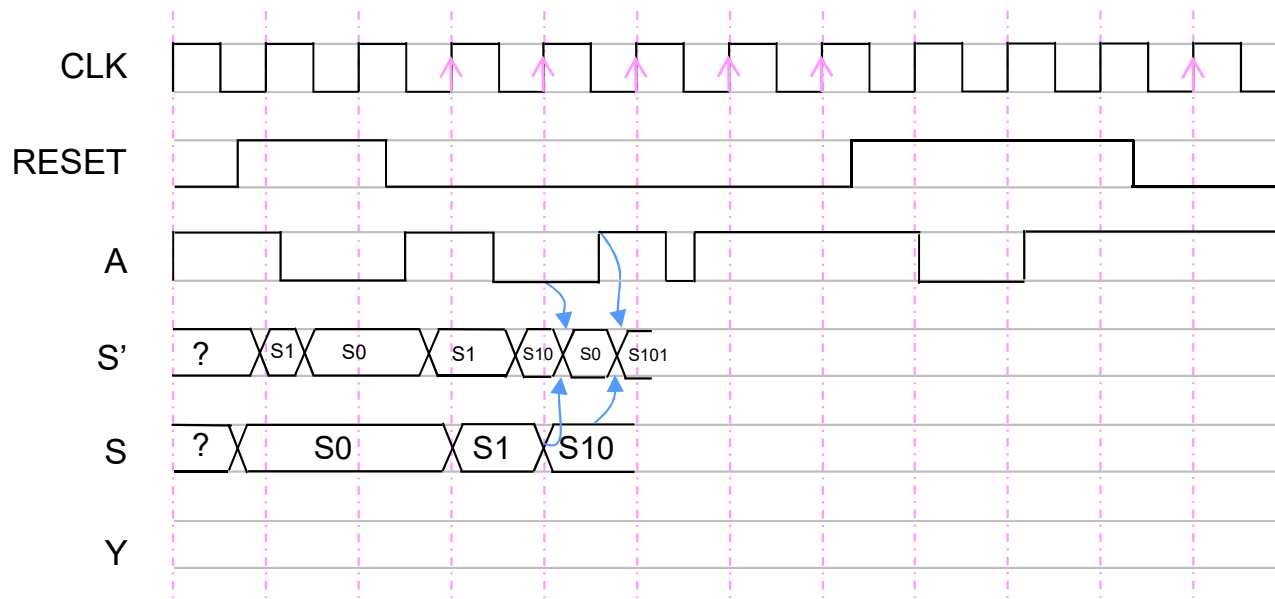
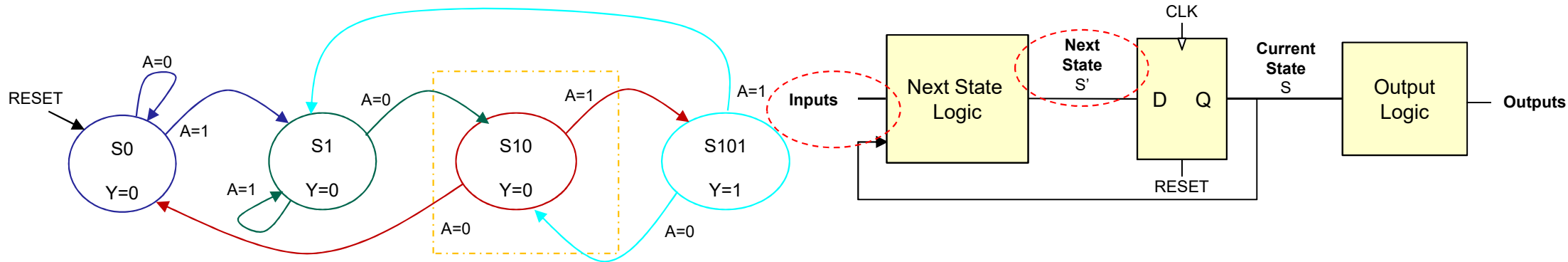
# FSM Timing Diagram: Drawing the timing diagram


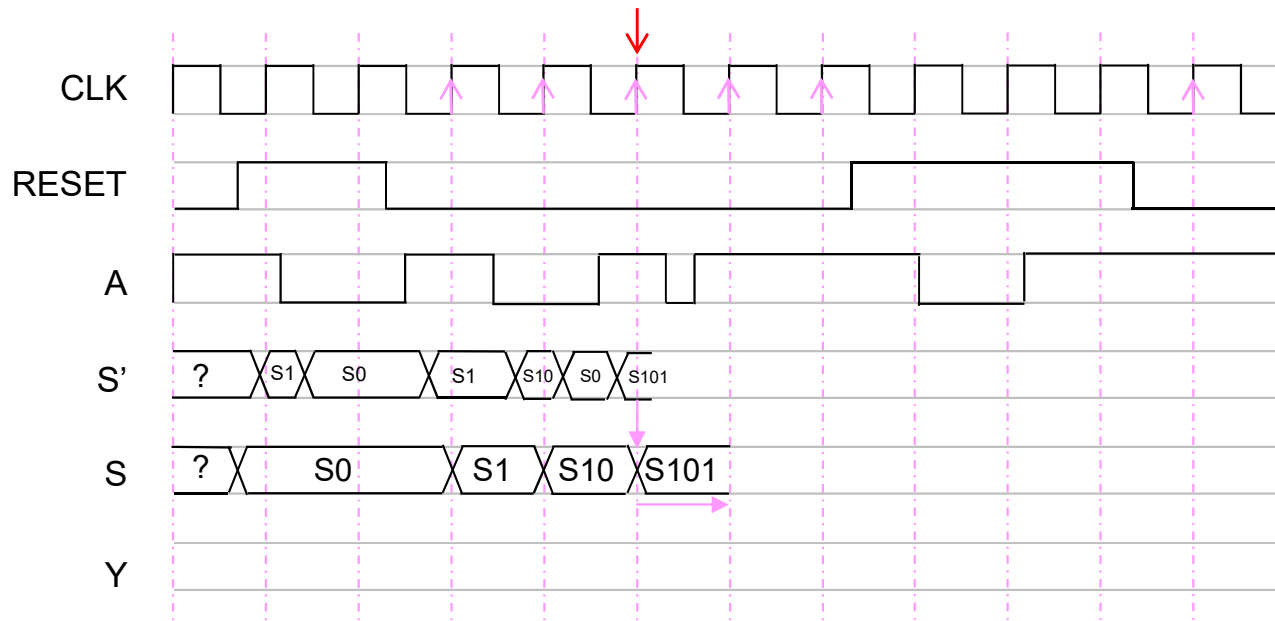  
# FSM Timing Diagram: Drawing the timing diagram





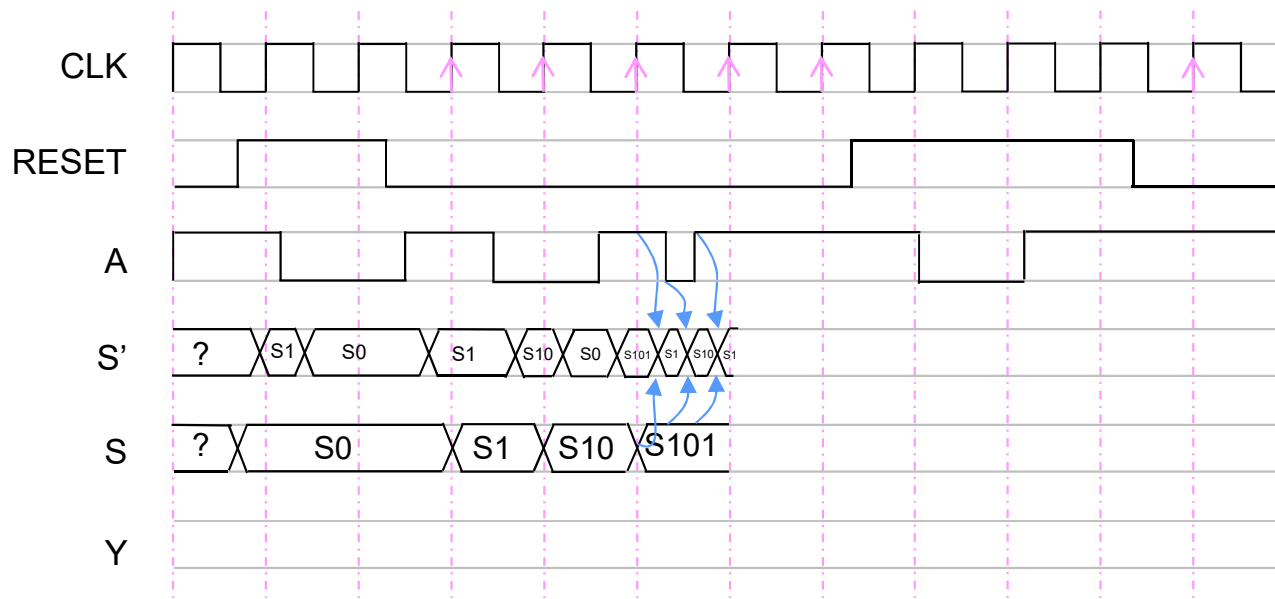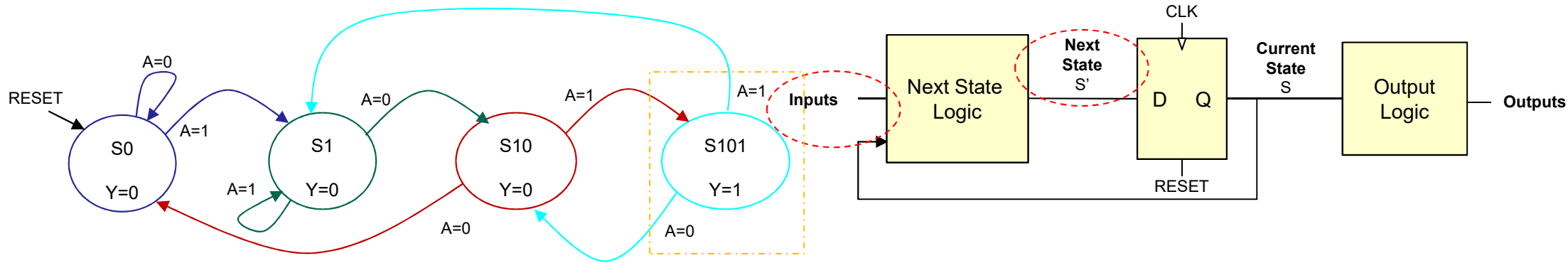
# FSM Timing Diagram: Drawing the timing diagram








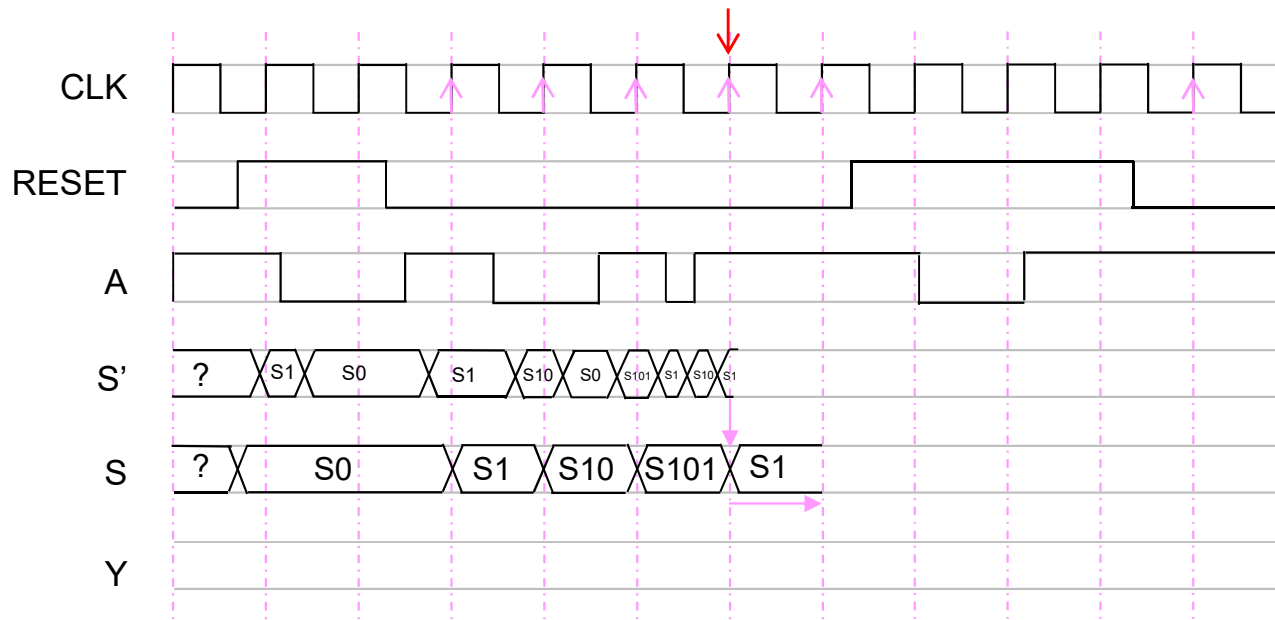
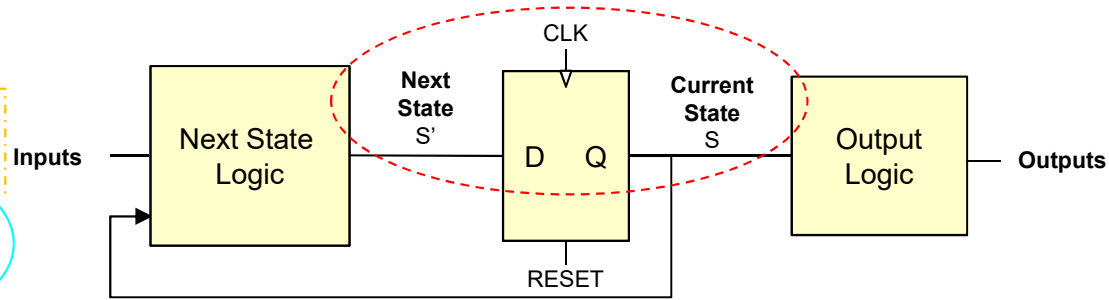
 
# FSM Timing Diagram: Drawing the timing diagram



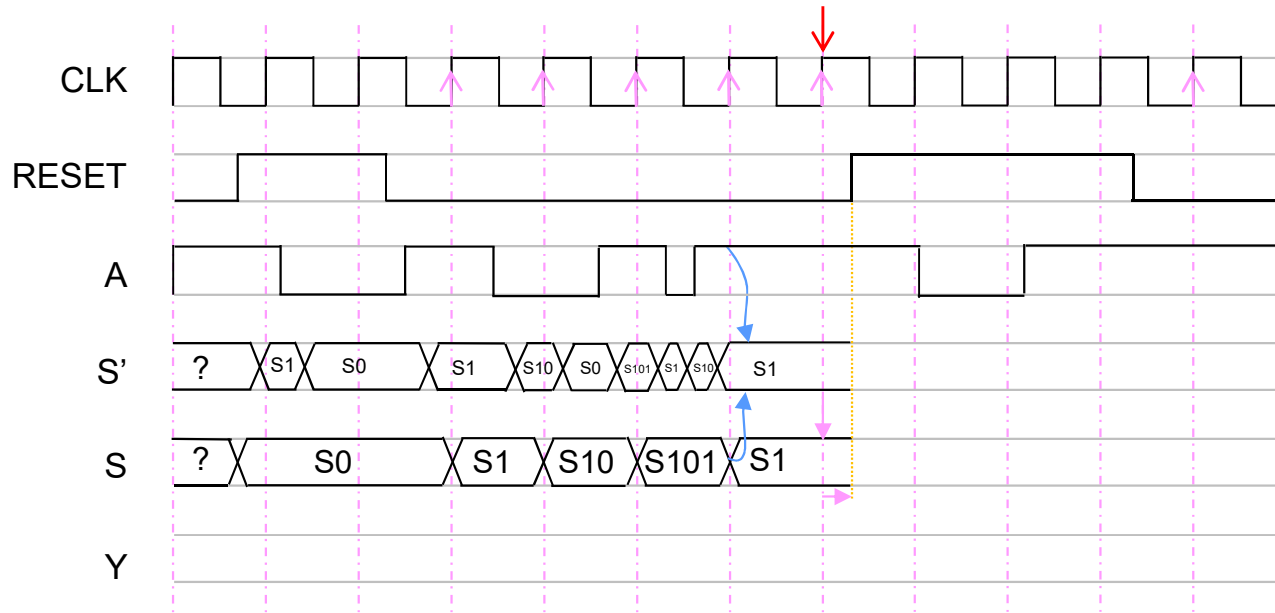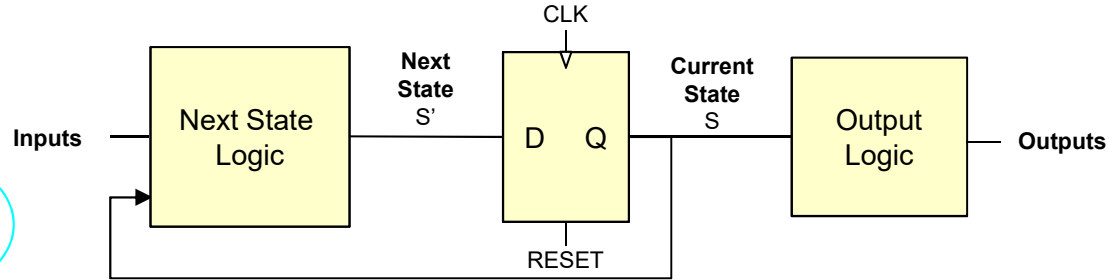
 
# FSM Timing Diagram: Drawing the timing diagram



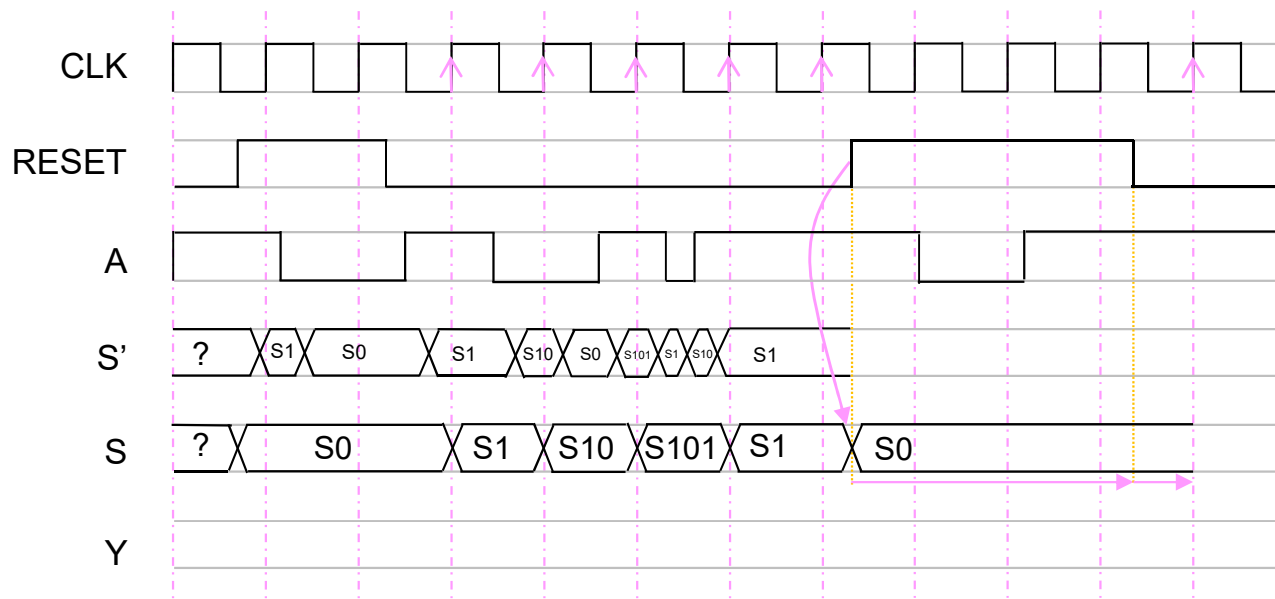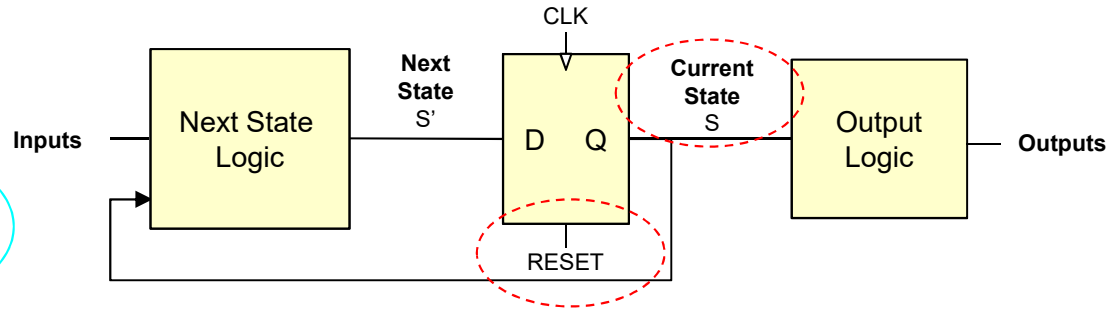
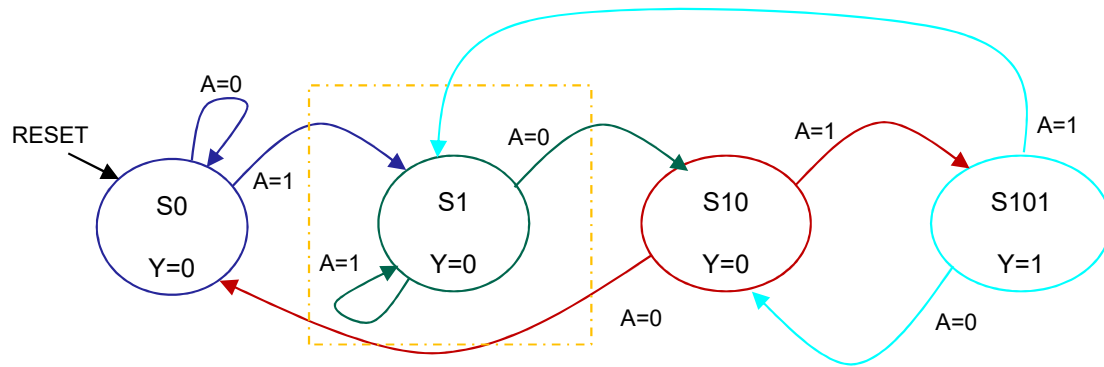
# FSM Timing Diagram: Drawing the timing diagram



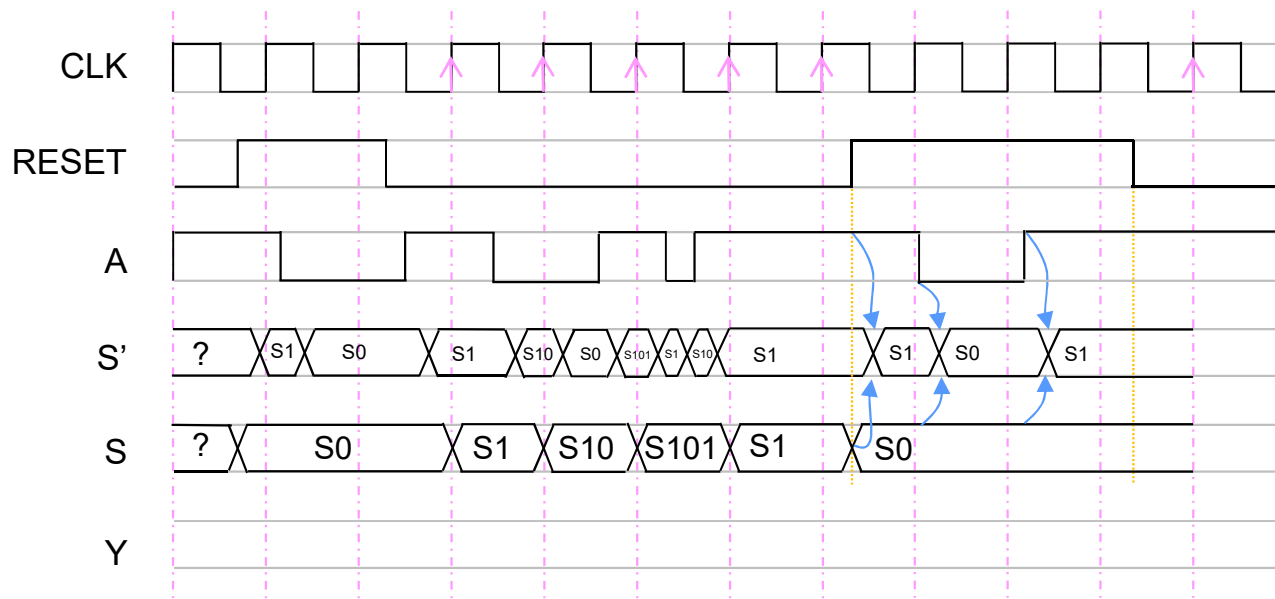
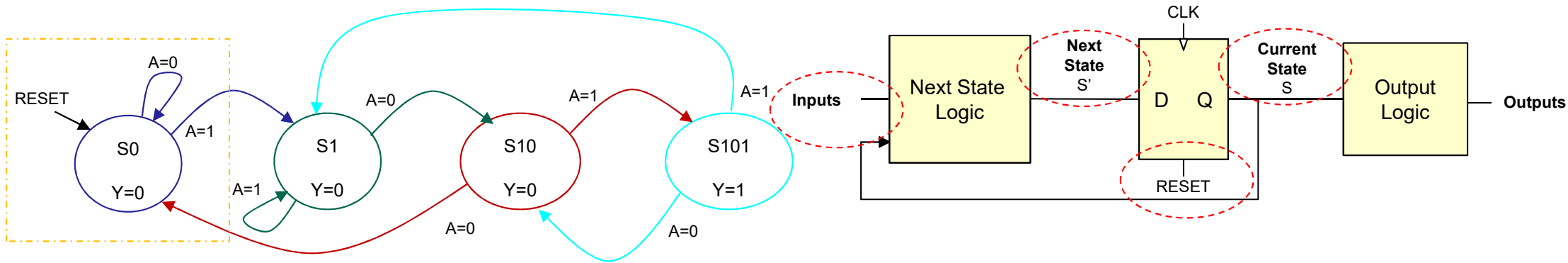
# FSM Timing Diagram: Drawing the timing diagram


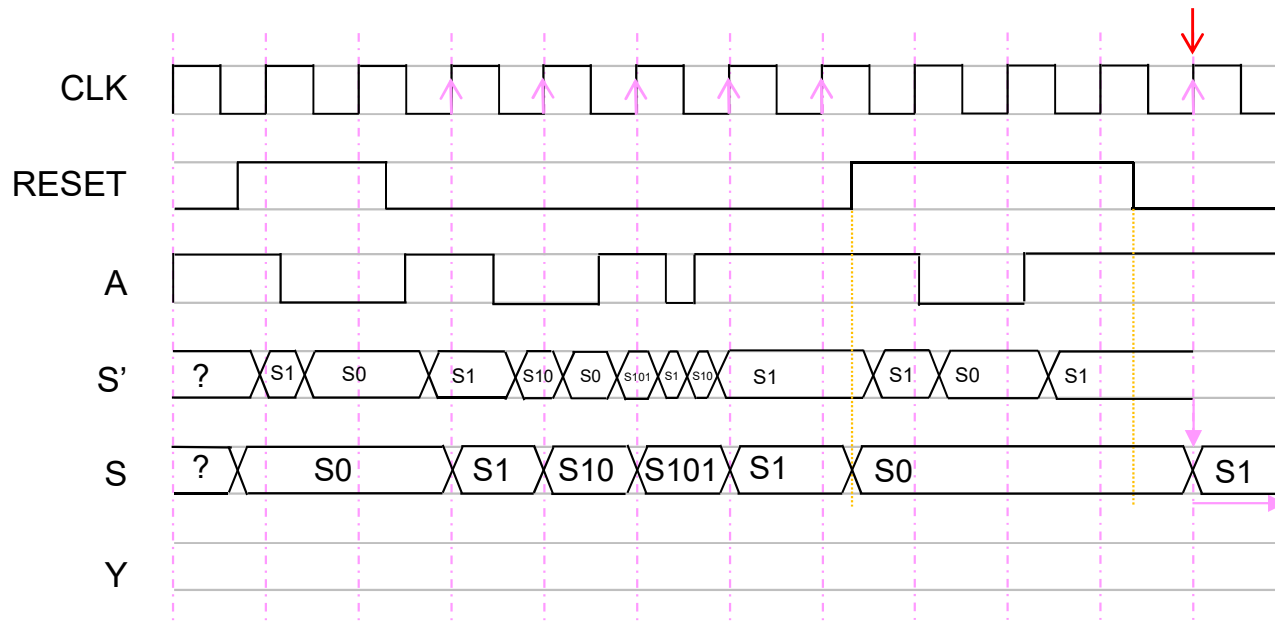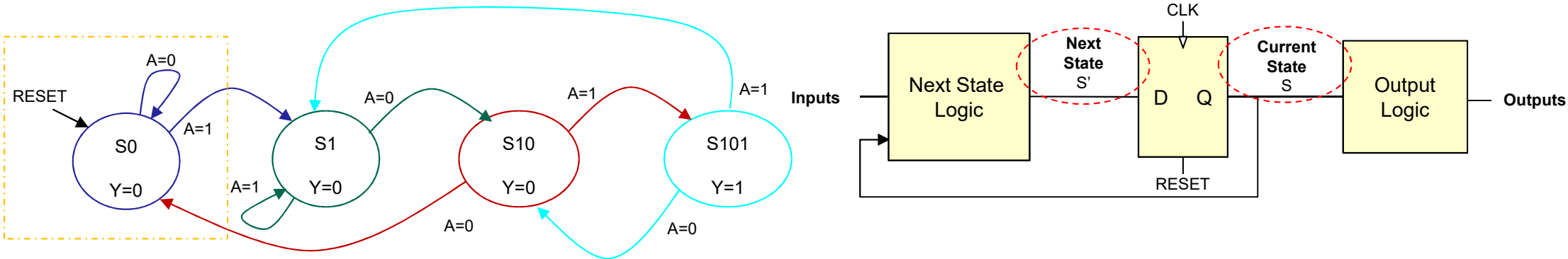
# FSM Timing Diagram: Drawing the timing diagram


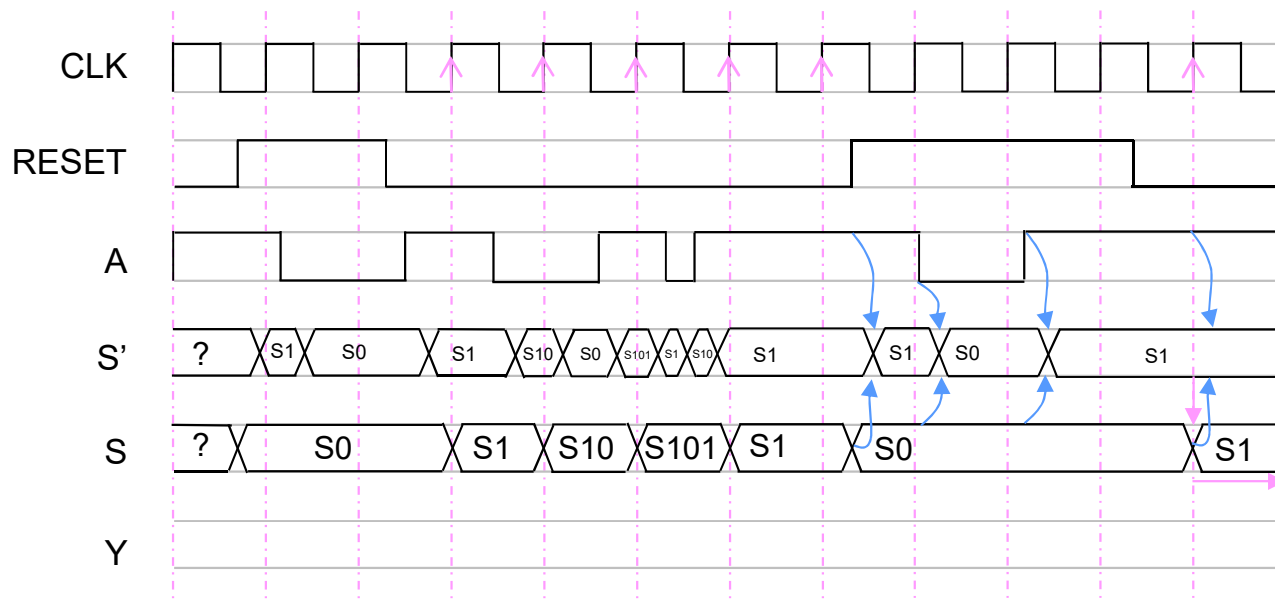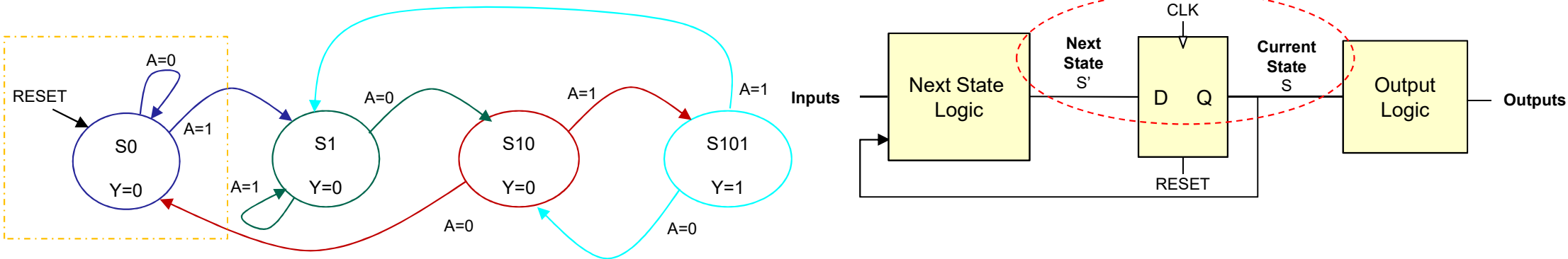
# FSM Timing Diagram: Drawing the timing diagram



# FSM Timing Diagram: Drawing the timing diagram

